

R16

Code No: 134CC

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year II Semester Examinations, December - 2019

PULSE AND DIGITAL CIRCUITS

(Common to ECE, ETM)

Time: 3 Hours

Max. Marks: 75

Note: This question paper contains two parts A and B.

Part A is compulsory which carries 25 marks. Answer all questions in Part A. Part B consists of 5 Units. Answer any one full question from each unit. Each question carries 10-marks and may have a, b, c as sub questions.

PART- A

(25 Marks)

- 1.a) Sketch the output response of RC high pass circuit for a pulse input. [2]
- b) Explain about RC low pass circuit as integrator. [3]
- c) Draw transient response of a diode clamping circuit. [2]
- d) Discuss the effect of diode characteristics on clamping voltage. [3]
- e) Draw diode as a switch circuit. [2]
- f) Discuss the applications of transistor. [3]
- g) List out the applications of Time base generators. [2]
- h) Define different sweep error. [3]
- i) Give the basic operational principles of sampling gates. [2]
- j) Compare RTL and DTL families. [3]

PART-B

(50 Marks)

- 2.a) Explain the operation of RC ringing circuit with help of circuit diagram.
- b) Derive an expression for the output levels under steady state conditions of a LP circuit excited by a ramp input. [5+5]

OR

- 3.a) Discuss the criteria for good differentiation and integration.
- b) Explain about uncompensated attenuators and how compensation is achieved. [5+5]
- 4.a) Draw the circuit of a clipping circuit with diode and explain.
- b) Draw a negative clamping and explain it. [5+5]

OR

- 5.a) Explain any two applications of voltage comparators.
- b) State and derive clamping circuit theorem. [5+5]

- 6.a) Explain how transistor acts as a switch? Design transistor switch circuit.
- b) Discuss about the piece-wise diode characteristics of a diode. [5+5]

OR

- 7.a) Discuss diode switching times in detail.
- b) Explain about SCS. [6+4]

8R 8R 8R 8R 8R 8R 8R 8R

8.a) Design Schmitt trigger. Explain its operation with help of circuit diagram and waveforms.

b) Explain the operation of a current sweep circuit with help of diagram and waveforms.

8R 8R 8R 8R **OR** 8R 8R [5+5] 8R 8R

9.a) Draw and explain the base and collector waveforms of a bistable multivibrator.

b) Explain the operation of Transistor Miller Time base generator. [5+5]

10.a) Realize 2-input NAND using TTL logic.

b) Realize the OR gate using discrete components. [5+5]

8R 8R 8R 8R **OR** 8R 8R 8R 8R [5+5] 8R 8R

11.a) Explain about DTL logic family in detail, with one example.

b) Compare TTL and MOS technologies.

---ooOoo---

8R 8R 8R 8R 8R 8R 8R 8R

8R 8R 8R 8R 8R 8R 8R 8R

8R 8R 8R 8R 8R 8R 8R 8R

8R 8R 8R 8R 8R 8R 8R 8R

8R 8R 8R 8R 8R 8R 8R 8R