

**CMR ENGINEERING COLLEGE: : HYDERABAD**  
**UGC AUTONOMOUS**  
**I-B.TECH-I-Semester End Examinations (Regular) - JULY- 2021**  
**BASIC ELECTRICAL ENGINEERING**  
**(Common to CSE, IT, CSD and CSC)**


[Time: 3 Hours]

[Max. Marks: 70]

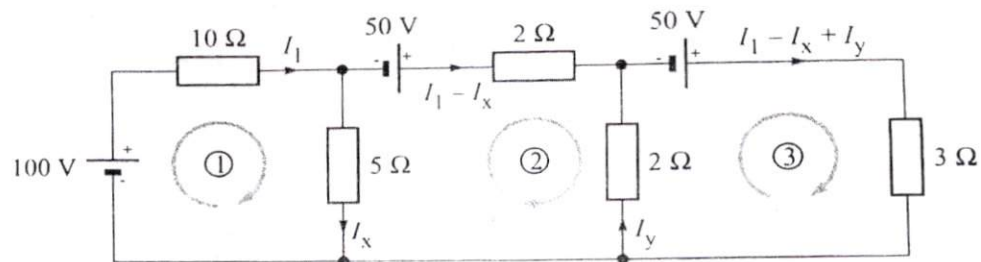1. Answer Any **FIVE** Questions. Each Question Carries 14 Marks
2. Illustrate your answers with NEAT sketches wherever necessary.

5 x 14M=70M

- 1 a) Using KVL, determine the currents  $I_x$  and  $I_y$  in the network shown in Fig.1.



- b) State and explain superposition theorem with an example.
- 2 a) Derive the expressions for average and RMS values of an alternating voltage wave  $v = V_m \sin \omega t$ .
- b) Derive the relation between phase and line quantities of voltage and current in a balanced three phase star connected load.
- 3 a) A 50 kVA, 1000/10000 V, 50Hz single phase transformer has iron loss of 1200W. The copper loss with 5 A in the high voltage winding is 500 W. Calculate the efficiency at i) 50%, ii) 75 % iii) 100 % of full load at 0.6 power factor.
- b) Discuss the various three phase transformer groups and their significance.
- 4 a) Explain the principle of production of rotating magnetic field in a 3-phase induction Motor
- b) Describe the construction of a DC machine and represent each part in it.
- 5 a) State and explain Kirchhoff Laws
- b) Two resistors of 4Ω and 2 Ω are connected in parallel to 10V DC source determine the current supplied by source and current in each resistor

- 6 a) A series RC circuit is excited with a DC voltage. Derive the expression for  $i(t)$  when the switch is closed at  $t=0$ .
- b) Obtain Norton's equivalent circuit with respect to the terminals AB for the circuit shown in Fig.2. Determine the current through a load resistor of  $5\Omega$ , if it were connected across terminals AB.

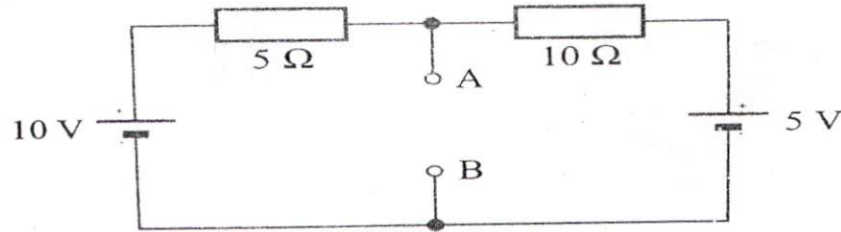


Fig.2

- 7 a) Draw and explain the torque-slip characteristics of a three phase induction motor.
- b) Derive the expression for resonant frequency in a series RLC circuit. A series RLC circuit consists of  $R=2\text{ ohm}$ ,  $L=2\text{mH}$  and  $C=0.6\text{ }\mu\text{F}$ . Determine the resonant frequency.
- 8 a) Compare two winding transformer and auto transformer.
- b) Calculate total energy consumed per day by the use of following loads:
- 6 number of 40 W lights operated 4 hours per day
  - 1 HP motor is operated 3 hours per day
  - 1 KW heater is operated 1 hour per day
  - 1 computer is used for 8 hours per day with printer about 30 minutes

\*\*\*\*\*