

Time: 3 hours

Max. Marks: 75

BR

BR

Answer any five questions
All questions carry equal marks

BR

BR

BR

- 1.a) Convert the decimal number 234 to binary, octal and hexadecimal number systems.

b) Find the canonical product-of-sums form for the function $F(x,y,z) = x'y' + z'x'$

c) Find the sum of $-8 + 2$ using signed 2's complement representation. (5+5+5)

- 2.a) Prove the following identity $xy + x'y' + yz = xy + x'y' + x'z$.

b) Simplify the given function $F(w, x, y, z) = \Sigma(0, 1, 2, 3, 4, 6, 7)$ to minimum number of literals. (6+9)

- 3.a) For the given function $F(w, x, y, z) = \Sigma(0, 1, 2, 3, 4, 6, 7, 9, 11, 15)$

i) Show the K-map

ii) Find all prime implicants and indicate which are essential.

iii) Find a minimal expression for F and realize using basic gates. Is it unique?

b) Design a 16x1 multiplexer using 4x1 multiplexers only. (10+5)

4. Use tabulation procedure to generate the prime implicants and essential prime implicants and to obtain all minimal expression for the given function $F(A, B, C, D) = \Sigma(1, 5, 6, 12, 13, 14) + d(2, 4)$. (15)

- 5.a) Define static hazard. Illustrate with example.

b) Design a combinational circuit that converts the given binary number to excess-3 code. (6+9)

- 6.a) Design a mod-10 counter using JK flip-flops.

b) Write the characteristic table, characteristic equations and excitation table for RS, T and D flip-flops. (7+8)

- 7.a) Illustrate the completely specified function with example. Write a procedure to design completely specified functions.

b) Define the terms primitive flow table and reduced flow table. (10+5)

BR

Write short notes on

- a) Incompletely specified functions
b) Asynchronous state machines
c) Logic synthesis. (5+5+5)

BR

BR

BR

---oo0oo---

BR

BR

BR